


## Self-Test

### True/False

1. A periodic waveform has a time period of 25ms and a pulse width of 5ms. The duty cycle is 20%.
2. Repeated division-by-10 is used to convert decimal numbers to binary numbers.
3.  $(11101000)_2$  is the 2's complement representation of -24.
4. The inputs to an AND gate are: A=1, B=0, C=1. The output will be LOW.
5. Full-adders can add two numbers and need not have a carry input or a carry output.
6. The look-ahead-carry adder is slower than the ripple-carry adder, since it requires additional logic circuits.
7. Full-adders can be used as a BCD-to-binary converter.
8. A multiplexer has multiple inputs and a single output.
9. Parity generators/checkers are useful because they do not require any additional data lines to function.
10. The commutative law of Boolean addition states that  $A+B=A B$

### Multiple Choice (单选题)

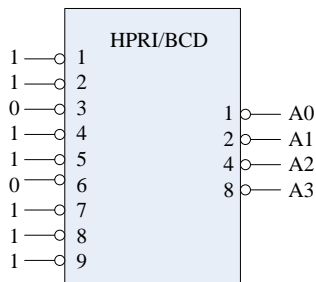1. Pulse width is defined as the\_\_\_\_\_
  - a. time that the pulse remains at the HIGH level.
  - b. time differential between the rising and falling edges.
  - c. length of the pulse measured at the LOW level.
  - d. duration of the pulse at the 50% level.
2. A negative-AND gate is functionally equivalent to a/an \_\_\_\_\_
  - a. AND gate with active-LOW inputs
  - b. NOR gate with active-LOW inputs
  - c. OR gate with active-LOW inputs
  - d. NOT gate with active-HIGH inputs
3. Which type of gate can be used to add two bits?
  - a. NAND
  - b. NOR
  - c. XOR
  - d. XNAND
4. What is one disadvantage of the ripple-carry adder?
  - a. The interconnections are more complex.
  - b. More stages are required to a full-adder.
  - c. It is slow, due to propagation time.
  - d. All of the above are correct.
5. The following figure shows a \_\_\_\_\_ and for the inputs shown, the outputs(A3,A2,A1,A0) will be\_\_\_\_\_.



- a. BCD-to-decimal decoder,1001
  - b. decimal-to-BCD priority encoder 0110
  - c. BCD-to-decimal decoder,0110
  - d. decimal-to-BCD encoder,1001
6. What is the decimal number for the BCD number, 10110110?
    - a. 182
    - b. 36
    - c. 116
    - d. Not a valid BCD number

7. Which of the following is not an important feature of the sum of products form of expressions?
  - a. All logic circuits are reduced to nothing more than simple AND and OR gates.
  - b. The delay times are greatly reduced over other forms.
  - c. No signal must pass through more than 2 gates, not including inverters.
  - d. The maximum number of gates that any signal must pass through is reduced by a factor of two.
8. A Karnaugh map will\_\_\_\_\_.
  - a. eliminate the need for tedious Boolean simplifications.
  - b. allow any circuit to be implemented with just AND and OR gates.
  - c. produce the simplest sum of products expression.
  - d. give an overall picture of how the signals flow through the logic circuit.

### Problems

1. Design a decoding circuit with three input lines, when inputs  $ABC=001, 011, 101, 111$ , the output is 1.

2. Try to implement the following logic function with a 4-16 decoder 74HC154 and logic gates.

$$F_1(A, B, C, D) = \sum m(0, 2, 4, 10, 11, 12, 13)$$

3. Please try to implement the following logic function with a 74HC151 and 74HC150:

$$F(A, B, C, D) = AB + CD$$