

电子技术

Introduction to Electronics

By Bao Qilian

鲍其莲

2018/10/111

电子技术

Chapter 5 Combinational Logic

Objective

- Gate circuits
- Basic Combinational logic circuits
  - AND-OR
  - AND-OR-Inverter
  - NAND/NOR
- Analyze and design of combinational logic circuits

Reading assignment

- P233-P255

2018/10/11

By Bao Qilian

2

Logic circuit

Combinational Logic circuit

组合逻辑电路

(无记忆功能)

Sequential Logic circuit

时序电路

(带存储元件, 有记忆)

2018/10/11

By Bao Qilian

3

电子技术

Basic Combinational Circuits

- AND-OR
- AND-OR-Invert
- XOR
- XNOR
- NAND
- NOR

2018/10/11

By Bao Qilian

4

1 AND-OR Logic

$X = AB + CD$

An AND-OR circuit directly implements **SOP** expression, assuming the complements of the variables are available.

A

B

C

D

&

&

≥1

X

ANSI standard distinctive shape symbols

ANSI standard rectangular outline symbols

2018/10/11

By Bao Qilian

5

Example chip: 74HC58

74HC58 (CMOS): dual AND-OR

- 1 two inputs AND-OR.
- 1 three inputs AND-OR

2

3

4

5

9

10

11

12

13

1

&

&

&

&

≥1

≥1

6

8

7

GND

14 V<sub>CC</sub>


2018/10/11

By Bao Qilian

6
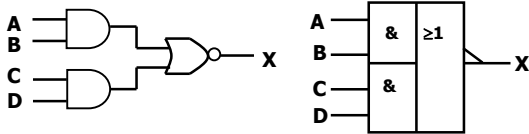
## 2 AND-OR-Invert Logic

$X = \overline{AB + CD} = (\overline{A} + \overline{B})(\overline{C} + \overline{D})$   
An AND-OR-Invert can be used to implement **POS** expression.




2018/10/11

By Bao Qilian

7
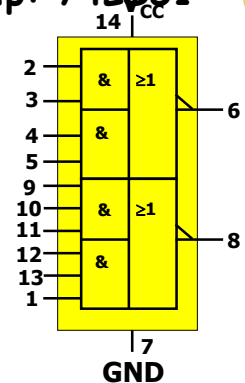
## Example chip: 74LS51

**74LS51** : dual  
2-wide AND-  
OR-Invert  
- 1 two inputs  
AND-OR-  
Invert.  
- 1 three inputs  
AND-OR-  
Invert



2018/10/11

By Bao Qilian

8

## 3 Exclusive-OR (XOR)

$$X = \overline{A}B + A\overline{B}$$



2018/10/11

By Bao Qilian

9

## 4 Exclusive-NOR (XNOR)

$$X = AB + \overline{A}\overline{B}$$




2018/10/11

By Bao Qilian

10
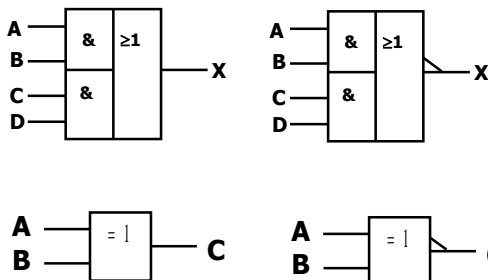
## 5 Combinational Logic Using NAND and NOR Gates

- NAND  $\overline{AB} = \overline{A} + \overline{B} \Rightarrow$  Negative-OR
- NOR  $\overline{A+B} = \overline{A}\overline{B} \Rightarrow$  Negative-AND



2018/10/11

By Bao Qilian

11

2018/10/11

By Bao Qilian

12

### The NAND Gate as a Universal Logic Element

- The NAND gate can be used to produce the NOT, AND, OR, and NOR operations.

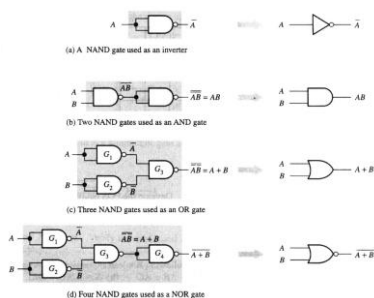


FIGURE 5-18  
Universal application of NAND gates.

13

### The NOR Gate as a Universal Logic Element

- The NOR gate can be used to produce the NOT, AND, OR, and NAND operations.

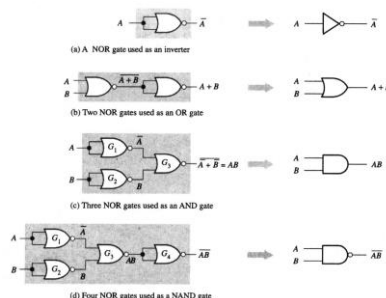


FIGURE 5-19  
Universal application of NOR gates.


14

**Example: Implementing the following expression using NAND gates:**

$$X = AB + CD$$

Solution:  $X = AB + CD$
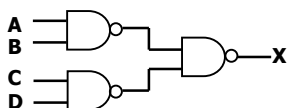
$$= \overline{\overline{AB} \cdot \overline{CD}} = \overline{\overline{AB} \cdot \overline{CD}}$$



2018/10/11

By Bao Qilian


15

**Example: Implementing the following expression using NOR gates:**

$$X = (A + B)(C + D)$$

Solution:  $X = (A + B)(C + D)$
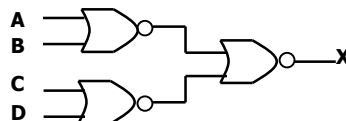
$$= \overline{\overline{(A + B)(C + D)}} = \overline{\overline{A + B} \cdot \overline{C + D}}$$



2018/10/11

By Bao Qilian

16

## Summary

- Basic combinational logic circuits
- Design of logic functions using basic logic circuits

2018/10/11

By Bao Qilian

17

Problems chapter 5:  
2, 6(d), 12(c),  
24(e), 26(g), 29.

18

By Bao Qilian