

# 电子技术 Introduction to Electronics

By Bao Qilian  
鲍其莲

2018/  
12/3 1

## Chapter 9 Shift Registers

### Objectives

- Registers
- Shift Registers
- Shift Register Counters
- Applications

### Reading assignments

- P481~P508

2018/12/3

By Bao Qilian

2

## 9.1 Register

- A *register* is a memory device that can be used to store more than one bit of information.
- A register is usually realized as several flip-flops with common control signals that control the movement of data to and from the register.

2018/12/3

By Bao Qilian

3

- A register is a generalization of a flip-flop. Where a flip-flop stores one bit, a register stores several bits
- The main operations on a register are the same as for any storage devices, namely
  - Load or Store: Put new data into the register
  - Read: Retrieve the data stored in the register (usually without changing the stored data)

2018/12/3

By Bao Qilian

4


### Control Signals

- When they are asserted, they initiate an action in the register
- *Asynchronous Control Signals* cause the action to take place immediately
- *Synchronous Control Signals* must be asserted during a clock assertion to have an effect

2018/12/3

By Bao Qilian


5

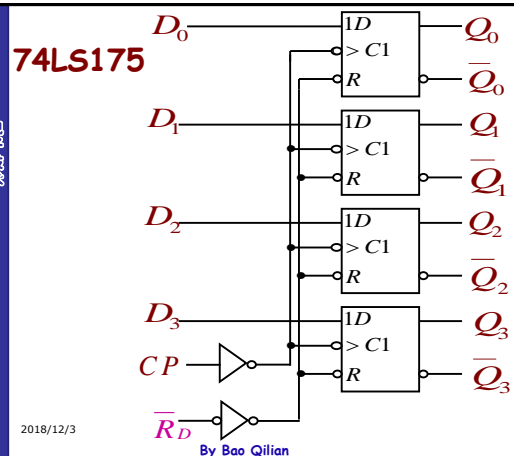

2018/12/3

By Bao Qilian

6




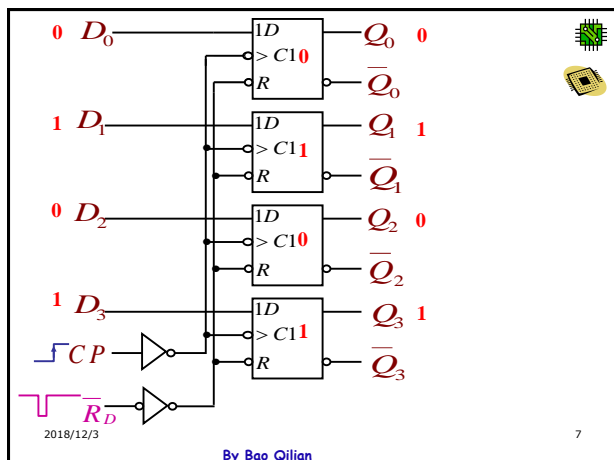






## Shift Registers

- A *shift register* has two basic functions:
  - Data storage
  - Data movement



2018/12/3

By Bao Qilian

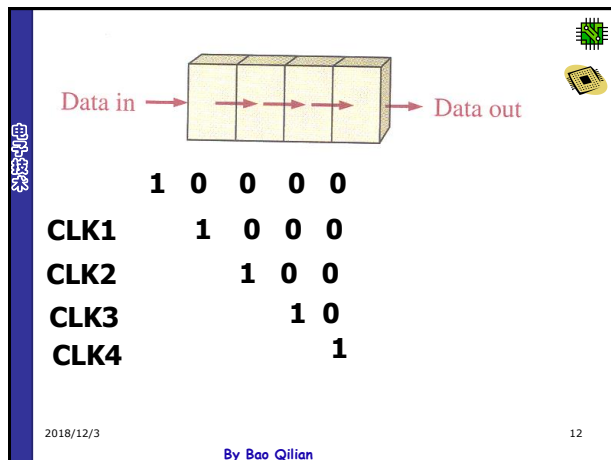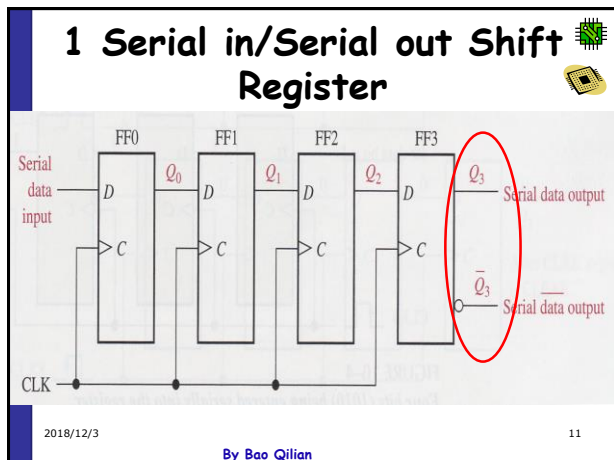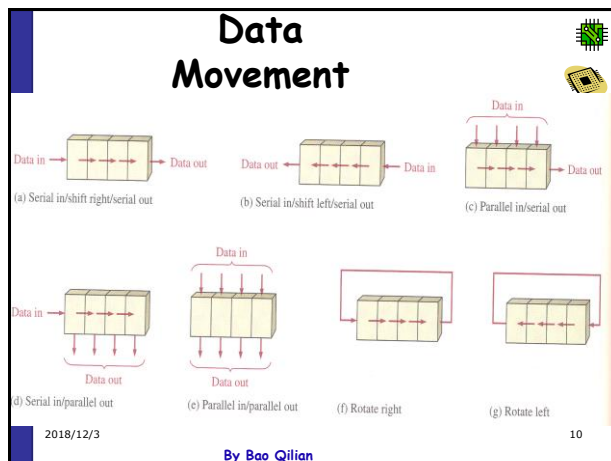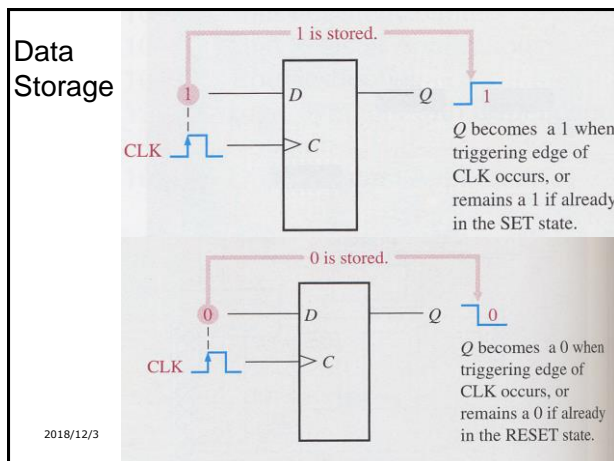


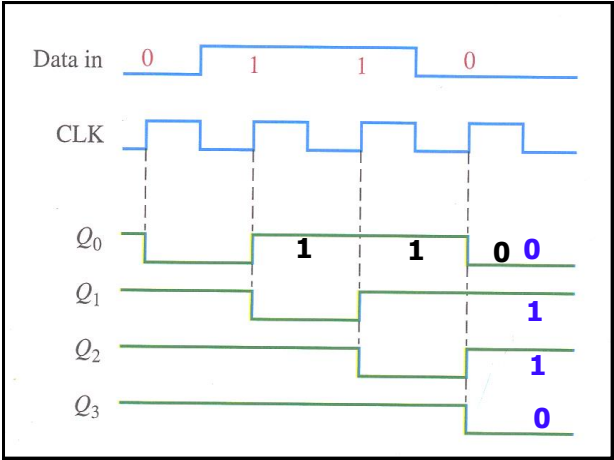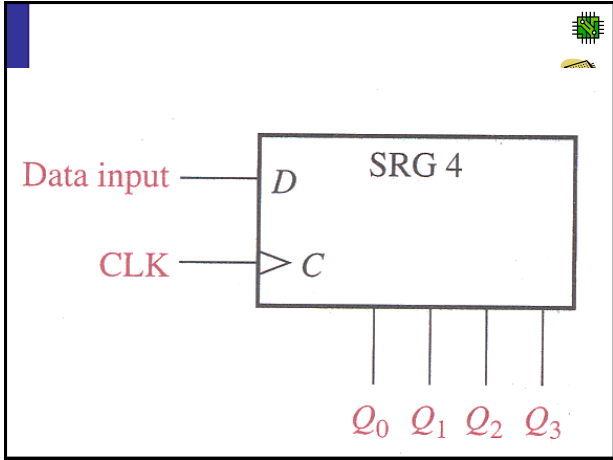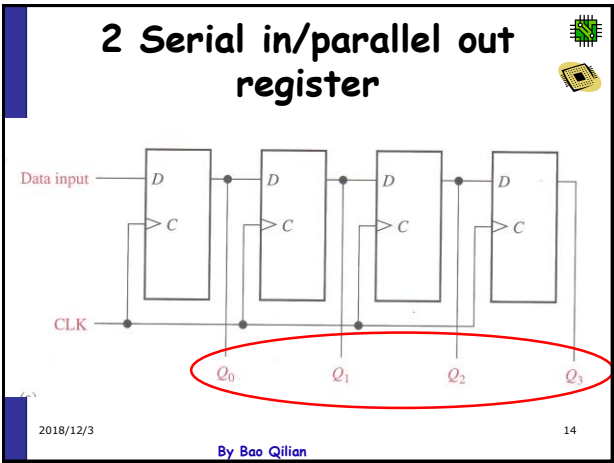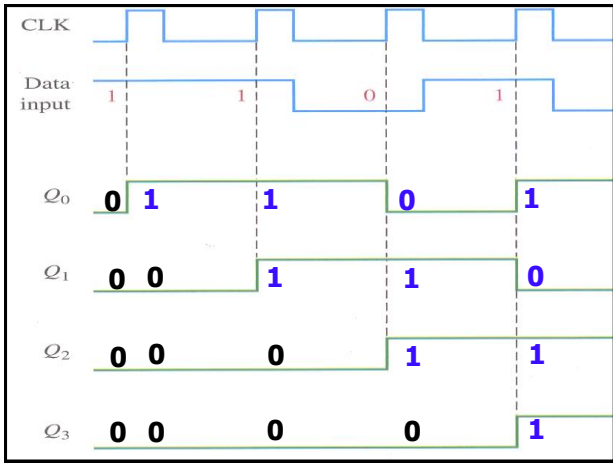

### 74HC164

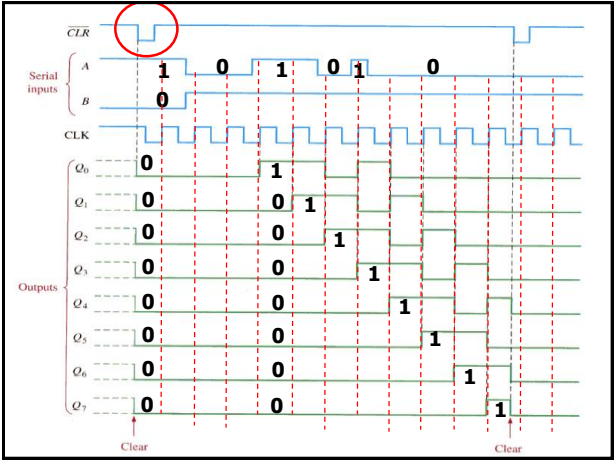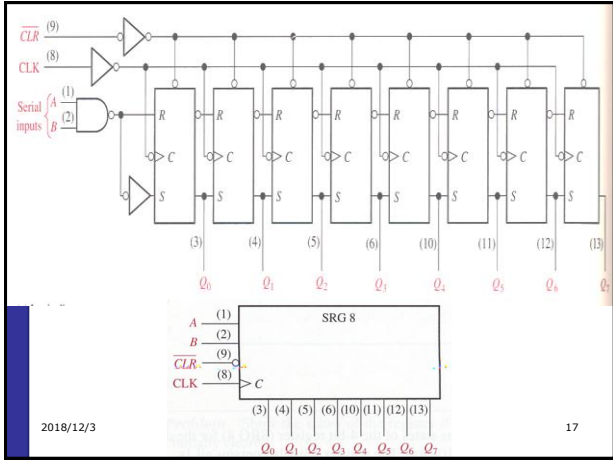



### 3 Parallel in/Serial out Register

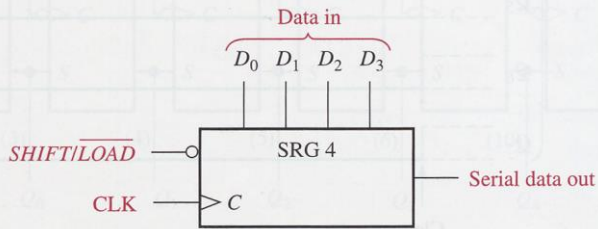


2018/12/3

By Bao Qilian

19

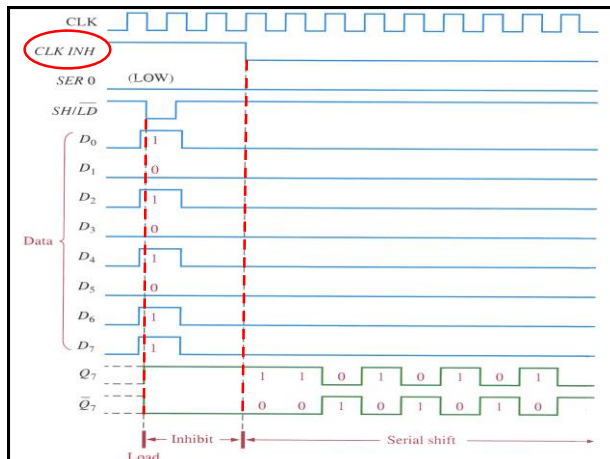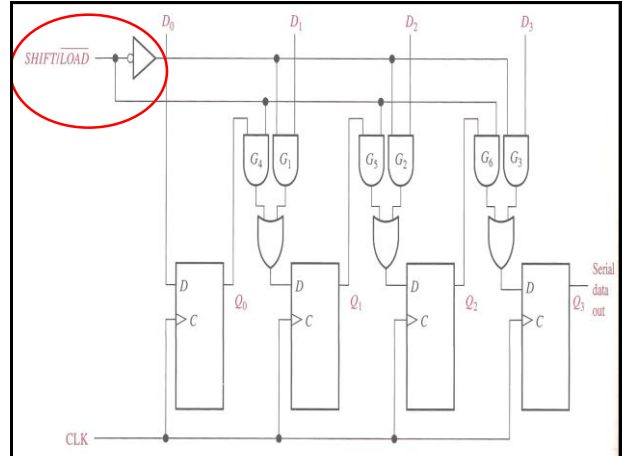


### 4 Parallel in/Parallel out register

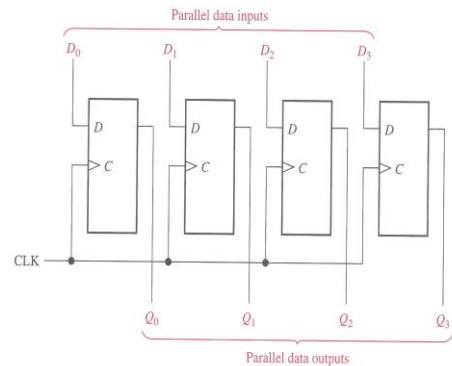

2018

### 4 Parallel in/Parallel out register

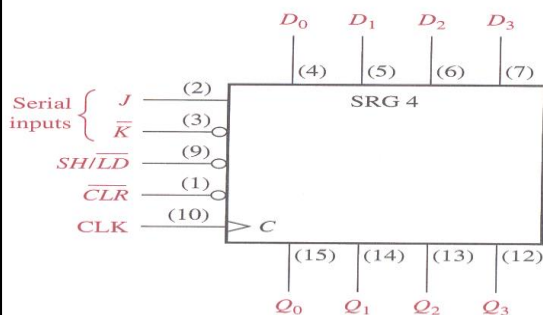

#### 74HC195: Function Table


This device is obsolete.

		INPUTS				OUTPUTS				
CLEAR	SHIFT/LOAD	CLOCK	SERIAL		PARALLEL				QA	QB
			J	K	A	B	C	D		
L	X	X	X	X	X	X	X	X	L	L
H	L	↑	X	X	a	b	c	d	a	b
H	H	L	X	X	X	X	X	X	QA	QB
H	H	↑	L	H	X	X	X	X	QA	QB
H	H	↑	L	L	X	X	X	X	L	QA
H	H	↑	H	H	X	X	X	X	H	QA
H	H	↑	H	L	X	X	X	X	QA	QA

$J = L, \bar{K} = L$   
 $J = H, \bar{K} = H$

$J = L, \bar{K} = H$   
 $J = H, \bar{K} = L$

By Bao Qilian

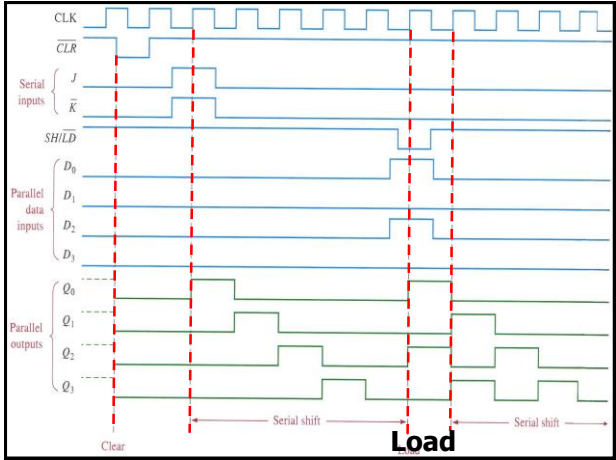

电子技术




# 5 Bi-directional Register

2018/12/3

By Bao Qilian

26

芯片图标

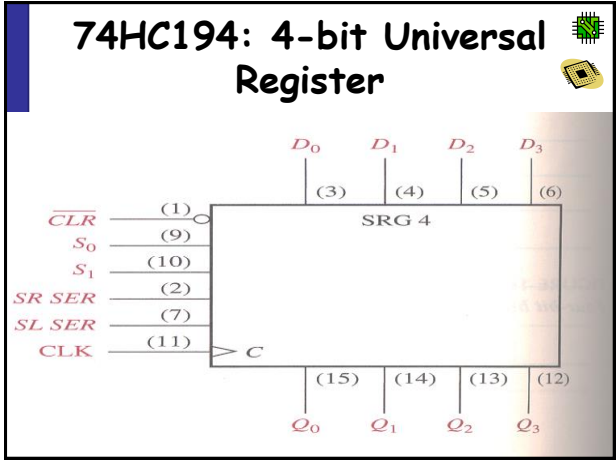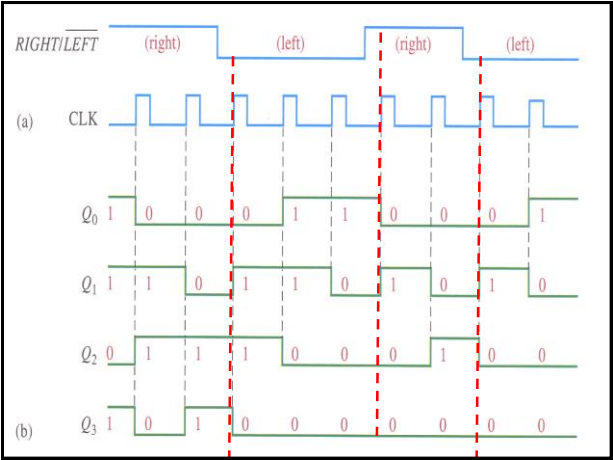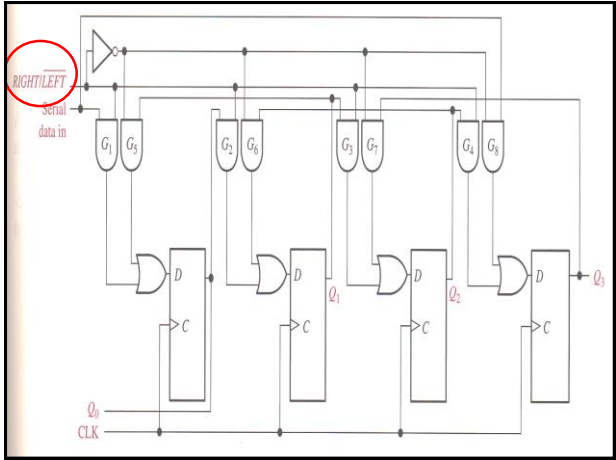

电子技术

# 74HC194: Function Table

S<sub>1</sub>S<sub>0</sub> Function

- S<sub>1</sub> and S<sub>0</sub> are mode control
- There are five possible operations


S <sub>1</sub>	S <sub>0</sub>	Function
0	0	inhibit
0	1	Shift right
1	0	Shift left
1	1	Load

operations

- Clear
- Parallel loading
- Right shifting
- Left shifting

CLR	S <sub>1</sub>	S <sub>0</sub>	CLK	SL	SER	SR	SER	D0	D1	D2	D3	Q0	Q1	Q2	Q3
L	X	X	X	X	X	X	X	X	X	X	X	L	L	L	L
H	X	X	L	X	X	X	X	X	X	X	X	Q0	Q1	Q2	Q3
H	H	H	↑	X	X	X	X	a	b	c	d	a	b	c	d
H	L	H	↑	X	r	X	X	X	X	X	X	r	Q0	Q1	Q2
H	H	L	↑	l	X	X	X	X	X	X	X	Q1	Q2	Q3	l
H	L	L	X	X	X	X	X	X	X	X	X	Q0	Q1	Q2	Q3

芯片图标

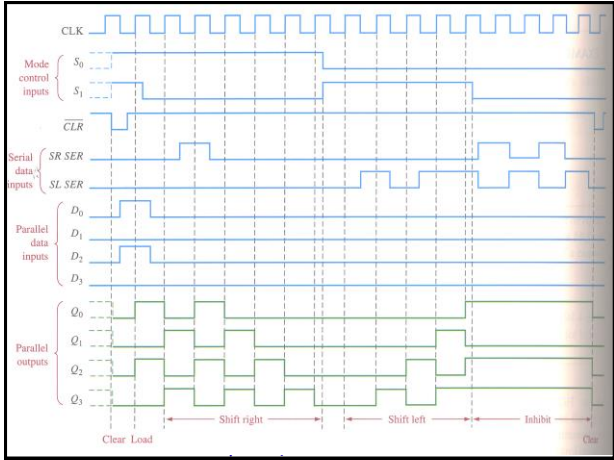

## 小结：移位寄存器

### 移位功能：

指寄存器里存储的代码能在移位脉冲的作用下依次**左移**或**右移**。

因此，移位寄存器不但可以用来**寄存代码**，还可以用来实现数据的**串行-并行转换**、**数值的运算及数据处理等**

2018/12/3

By Bao Qilian

32

## 9.2 Shift Register Counter (移位寄存器型计数器)

### Shift Register Counter


- **Johnson Counter** (扭环型计数器) : the complement of the output of the last FF connected back to the first FF
- **Ring Counter** (环型计数器) : the output of the last FF connected back to the first FF

2018/12/3

By Bao Qilian

33

## 1 Johnson Counter

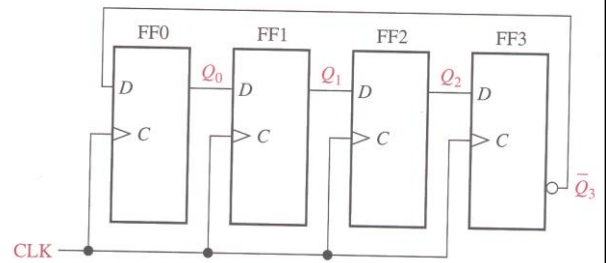

2018/12/3

By Bao Qilian


34

Clock Pulse	$Q_0$	$Q_1$	$Q_2$	$Q_3$
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1







2018/12/3

By Bao Qilian

35

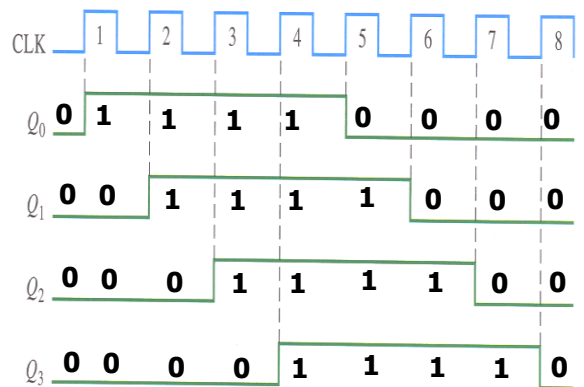



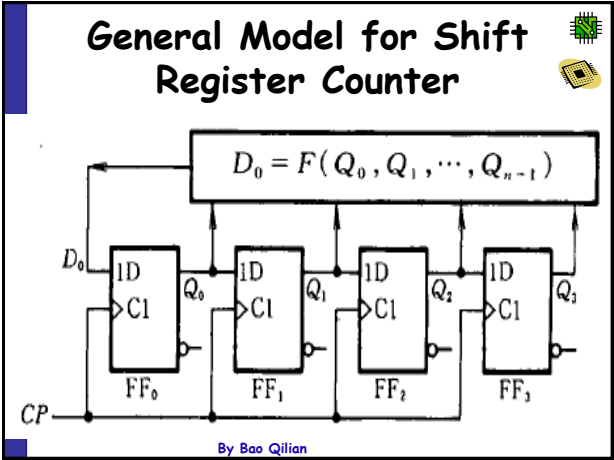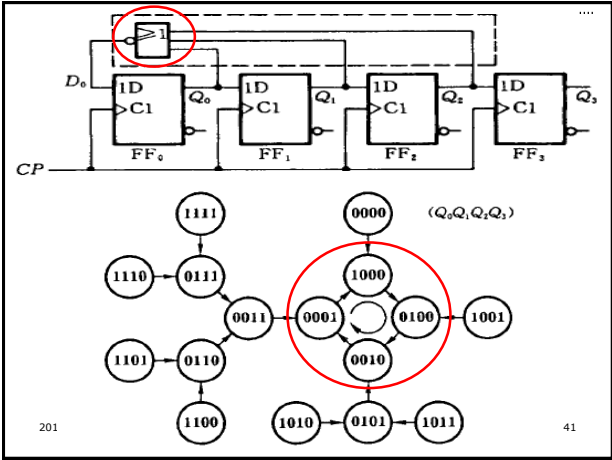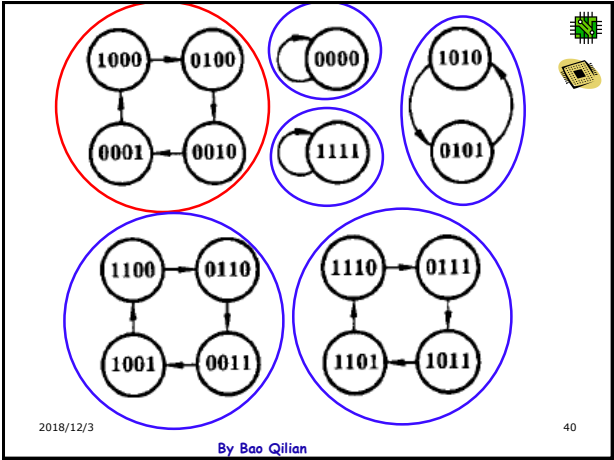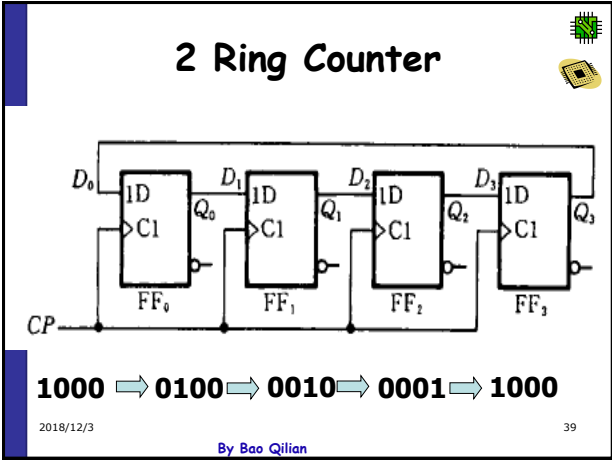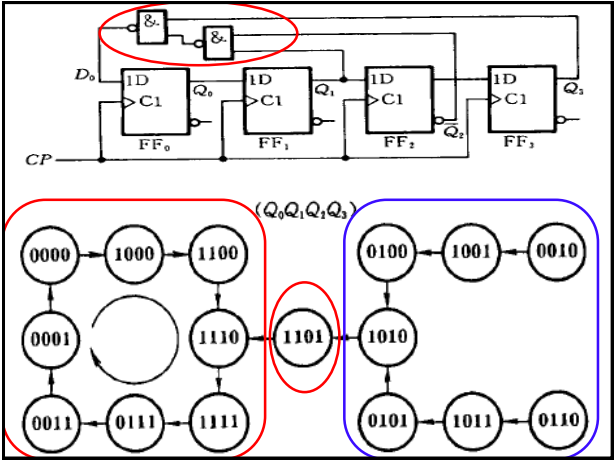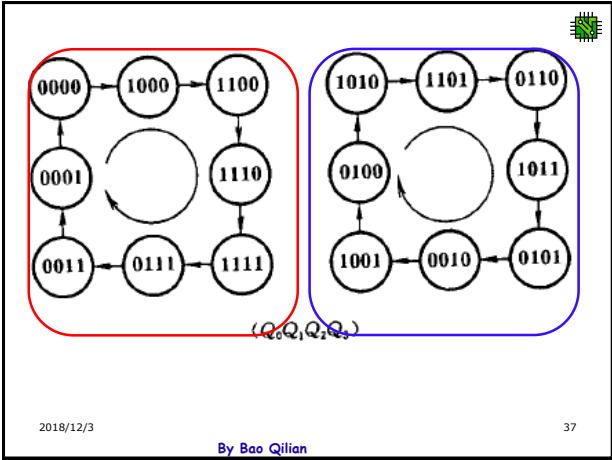


## 9.3 Applications of Shift Register Counters

2018/12/3

By Bao Qilian

43

## Time Delay

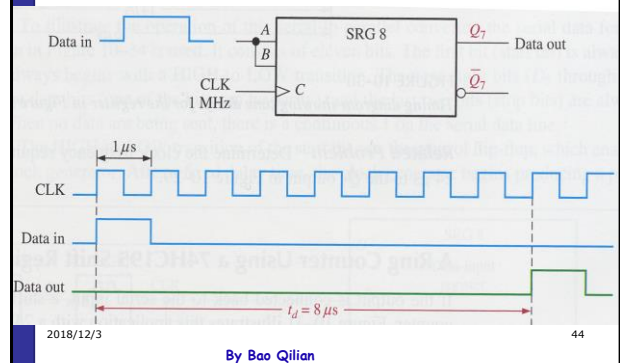

2018/12/3

By Bao Qilian

44

For output  $Q_i$ :  
Time delay  $= (i+1) \times \text{Period}_{\text{CLK}}$


e.g.  $Q_1$ :

$$\begin{aligned} \text{Time delay} &= (1+1) \times \text{Period}_{\text{CLK}} \\ &= 2 \times \text{Period}_{\text{CLK}} \\ &= 2 \times 1/1\text{MHz} \\ &= 2 \times 1\mu s \\ &= 2 \mu s \end{aligned}$$

2018/12/3

By Bao Qilian

45

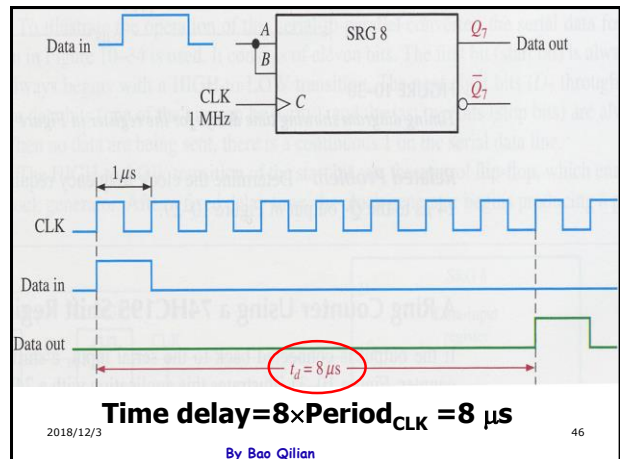


2018/12/3

By Bao Qilian

46
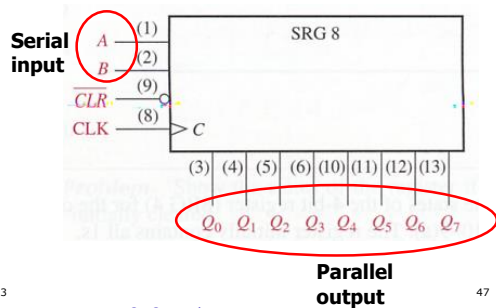
## 74HC164: 8-Bit serial in/parallel out shift register




2018/12/3







By Bao Qilian




47
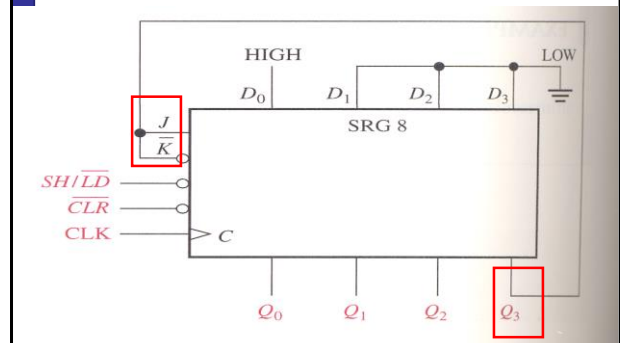
## 2 Ring Counter Using 74HC195 (4-bit shift register)





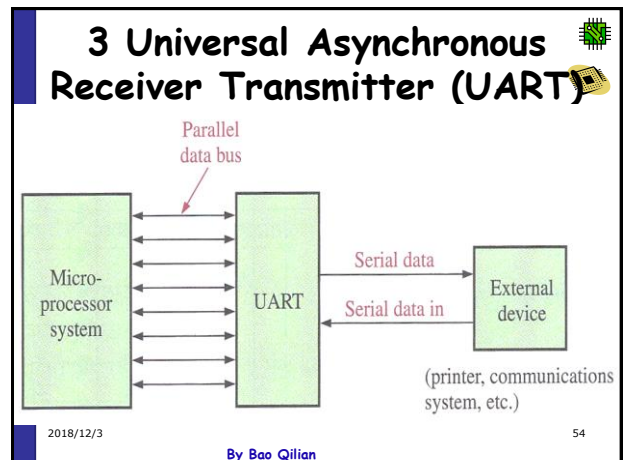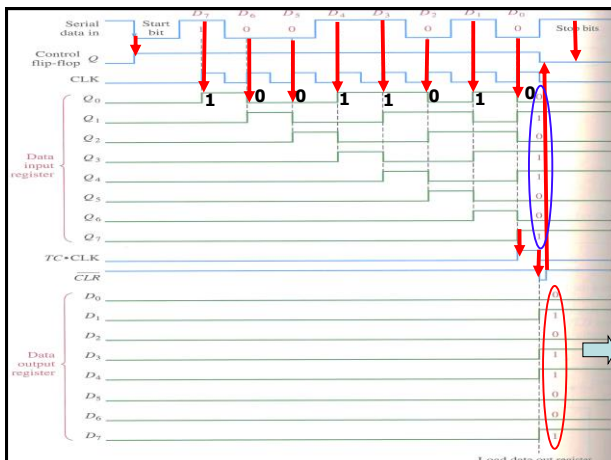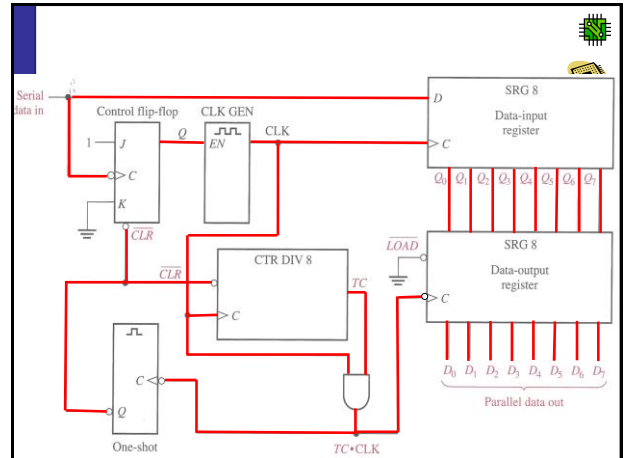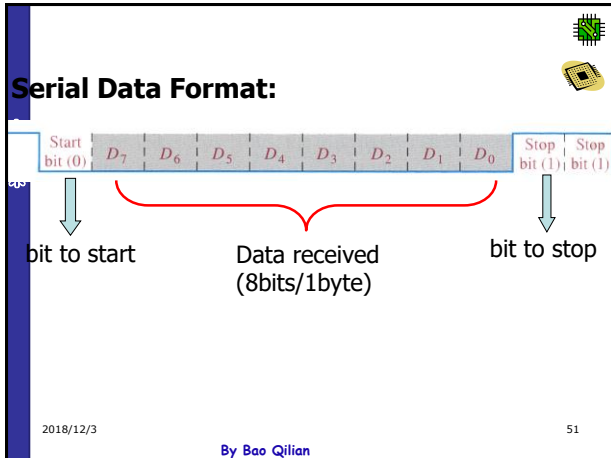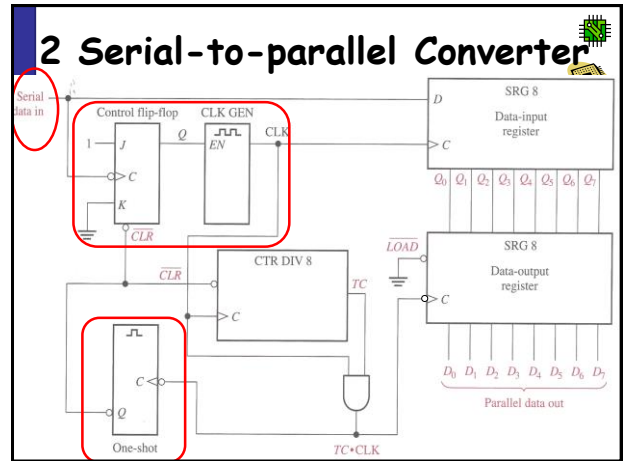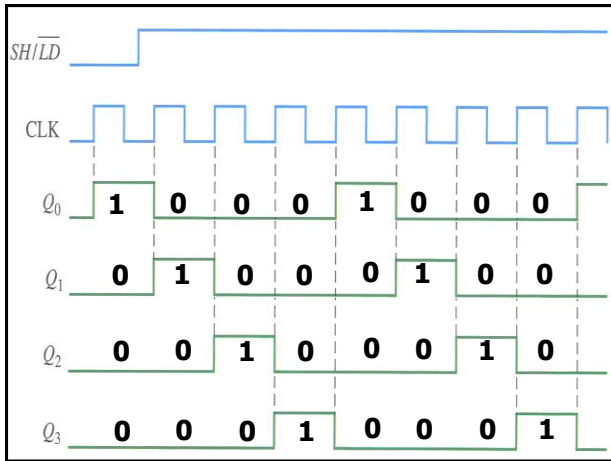

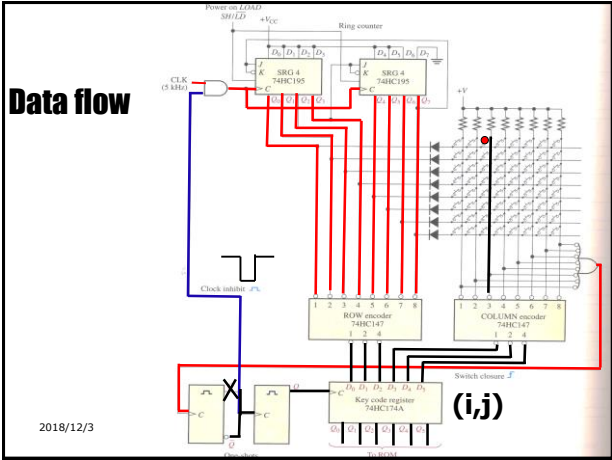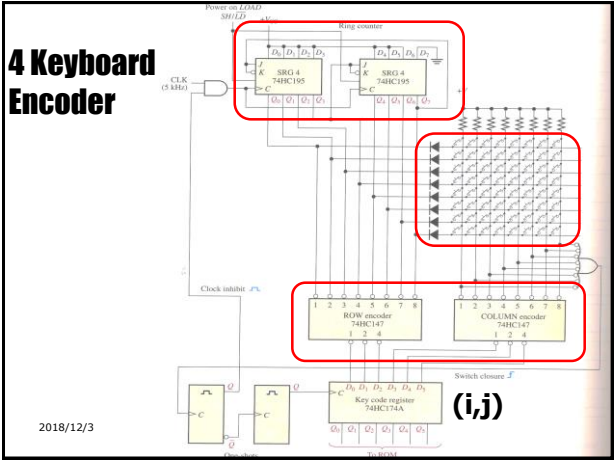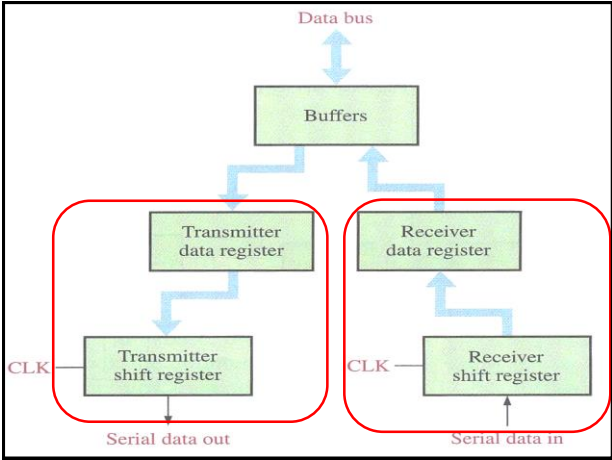

## Summary

- **Registers:** storage
- **Shift Registers:** storage+movement
  - Serial in/serial out
  - Serial in/parallel out
  - Parallel in/parallel out
  - Parallel in/serial out
  - Bidirectional shift register
- **Shift Register Counters**
  - Johnson shift register counter
  - Ring counter
- **Applications**

2018/12/3

By Bao Qilian