 


MSI	RESET	LOAD	MODULE					
CHIP	(清零)	(置数)	(进制)					
74LS160	异步	同步	10					
	Asynchronous	Synchronous						
74LS161	异步	同步	16					
	Asynchronous	Synchronous						
74LS163	同步	同步	16					
	Synchronous	Synchronous						
74LS190	无	异步	(加/减)10					
	none	Asynchronous	Up/down 10					
74LS191	无	异步	Up/down					
	none	Asynchronous	16					
By Bao Qilian								




Synchronous Sequential Circuit Models:



· Structural

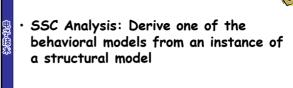- Logic diagram
- Excitation Equations
- Output equations
- · Behavioral
 - Transition and output equations
 - Transition table
 - State table (Next-state table)
- -State diagram (graph)




· SSC Design : Derive a structural model from one of the behavioral models

2018/12/3

By Bao Qilian

 Analysis of Synchronous Sequential Circuits Step1: Derive the excitation and output



equations

Step2: Derive the transition equations Step3: Construct the transition table


Step4: Construction the next-state

table

Step5: Draw state diagram

2018/12/3

By Bao Qilian

 

Step1: Derive the excitation and output equations



Excitation equation:

$$\boldsymbol{J}_0 = \overline{\boldsymbol{X}} + \overline{\boldsymbol{Q}}_1$$

$$K_0 = 1$$

$$\boldsymbol{J}_1 = \boldsymbol{Q}_0$$

$$\boldsymbol{K}_{1} = \boldsymbol{X} + \boldsymbol{Q}_{0}$$

Output equation:

$$Y = X\overline{Q}_0Q_1 + \overline{X}Q_0Q_1$$

2018/12/3

By Bao Qilian

Step2: Derive the transition equations



42

- · Use the characteristic equation for J-K flip-flops: $Q^{n+1} = J\overline{Q} + \overline{K}Q$
- ☐ The resulting transition equations are: $Q_0^{n+1} = J_0 \overline{Q}_0 + \overline{K}_0 Q_0 = (\overline{X} + \overline{Q}_1) \overline{Q}_0 + 0 \cdot Q_0$ $= \overline{X}\overline{Q}_0 + \overline{Q}_0\overline{Q}_1$ $Q_1^{n+1} = J_1\overline{Q}_1 + \overline{K}_1Q_1 = Q_0\overline{Q}_1 + \overline{X+Q_0}Q_1$

2018/12/3

 $= Q_0 \overline{Q}_1 + \overline{X} \overline{Q}_0 Q_1$ By Bao Qilian

Step3: Construct the transition table X=0X=1 Q_1^{n+1} Q_0^{n+1} Q_0^{n+1} Υ Q_1^{n+1} Υ $Q_1 Q_0$ 0 0 0 1 0 0 1 0 1 0 1 1 0 0 1 0 0 2 1 0 1 1 0 0 0 1 3 0 1 1 0 0 0 0


By Bao Qilian

Step4: Construction the next-state table



	X=0		X=1			
Q	Q	Y	Q	Y		
0	1	0	1	0		
1	2	0	2	0		
2	3	0	0	1		
3	0	1	0	0		
2018/12/3 44						

2018/12/3 By Bao Qilian

 

同步时厚逻辑电路的分析方法

分析一个时序电路,就是要找出给定电路的逻辑 🥟 功能(状态表、状态图或时序图)。



一般步骤:

1. 写方程式

时钟方程: 各个触发器时钟信号的逻辑表达式; 输出方程: 时序电路各个输出信号的逻辑表达式 驱动方程: 各个触发器同步输入端信号的逻辑表达式

2. 求状态方程

把驱动方程代入相应触发器的特性方程即可求出

By Bao Qilian

3. 进行计算

把电路输入和现态的各种可能取值,代入状态方程 和输出方程进行计算,求出相应的次态和输出方程 注意事项:

- 状态方程有效的时钟条件,凡不具备时钟条件者
- 触发器将保持原状态不变;
- 电路的现态:
- 不能漏掉任何可能出现的状态和输入的取值;
- 若给定了起始值,可从给定起始值开始依次计算
- 否则可自设起始值。

2018/12/3

By Bao Qilian

4. 画状态图或列状态表、画时序图



48

注意事项:

- 状态转换是由现态转换到次态;
- 输出是现态和输入的函数:
- 画时序图时注意时钟条件。
- 5. 说明电路功能

2018/12/3

47

By Bao Qilian

